
January 28, 2020


${\bf ASSIGNMENT~1-Measuring~Voltages}$

1)	46.4 Ω at the RS-12 multimetre	
2)	46.4 Ω at the NI elvis digital multimetre	
3)	1.28 %	
4)	$4.93~ extbf{\emph{V}}$	
5)	$4.92~ extbf{\emph{V}}$	
6)	0.20 %	
7)	$5.0055~oldsymbol{V}$	
8)	$5.0083~ extbf{\emph{V}}$	
9)		

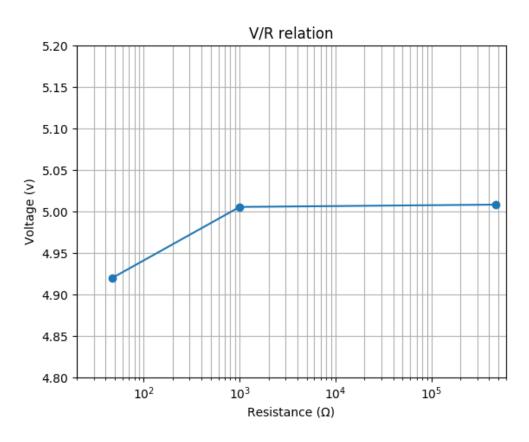


10) $9 \mu A$

11)

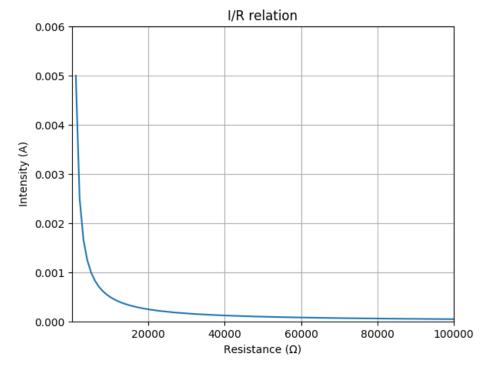


12) 19 $k\Omega$

13)

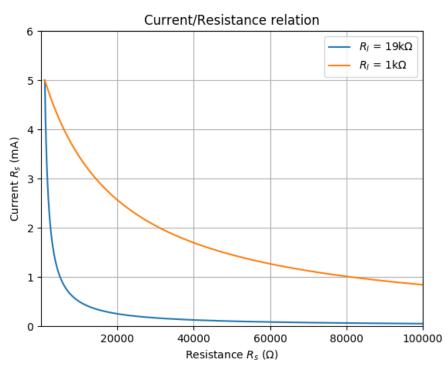

Resistance R_s (Ω)

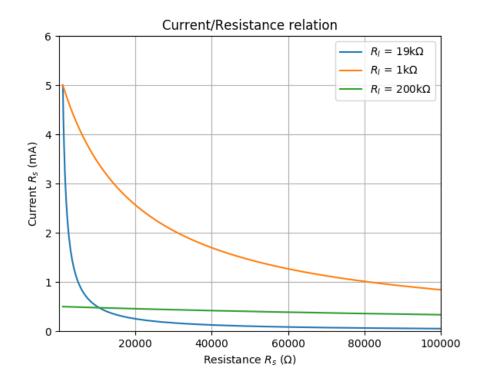

Submitted by Rolf Vidar Hoksaas with Jonatan H. Hansen on January 28, 2020.

3