

March 6, 2020

ASSIGNMENT 3 — RC filter

“ Find $H(j\omega)$ for a low-pass RC filter of the type illustrated in the figure. ”

Since the impedance Z_C of the condensator equals $\frac{1}{j\omega C}$, can we insert it into the expression:

$$\begin{aligned} V_{out} &= \frac{Z_C}{R + Z_C} \cdot V_{in} \\ V_{out} &= \frac{1}{R/Z_C + 1} \cdot V_{in} \\ V_{out} &= \frac{1}{R \cdot j\omega C + 1} \cdot V_{in} \end{aligned}$$

We therefore know the frequency response is $H(j\omega) = \frac{1}{1+j\omega RC}$. □

“ Find the the expression describing the relationship between the amplitude of the input voltage V_{in} and the amplitude of the output voltage V_{out} of the RC filter as a function of frequency. ”

The relationship between the output value of the voltage and its input is given by

$$\begin{aligned} V_{out}(t) &= |H(j\omega)| \cdot V_{in}(\omega, t) \\ V_{out}(t) &= |H(j\omega)| \cdot \cos(\omega t + \phi_c) \\ V_{out}(t) &= \frac{1}{\sqrt{1 + (\omega RC)^2}} \cdot \cos(\omega t + \angle H(j\omega)) \\ V_{out}(t) &= \frac{1}{\sqrt{1 + (\omega RC)^2}} \cdot \cos(\omega t + \arctan(\omega RC)) \end{aligned}$$

and we know the boundaries of the cosinus is ± 1 , therefore the amplitude is given by

$$A_{out} = |H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

□

“ Assume $C = 22nF$, and that we want the cutoff frequency of the filter to be $200Hz$. Find R . The cutoff frequency is defined as the frequency where the amplitude of the output signal is $1/\sqrt{2} \approx 0.7071$ times the amplitude of the input signal. ”

Given

$$H(j\omega) = \frac{1}{\sqrt{1 + j\omega RC}}$$

and the definition of cutoff frequency (where the cutoff frequency is $1/\sqrt{2}$ the DC voltage, thereby the frequency being ω_c .)

$$\begin{aligned} |H(j\omega_c)| &= \frac{1}{\sqrt{1 + (\omega_c RC)^2}} = \frac{1}{\sqrt{2}} H(j0) \\ \Rightarrow \frac{1}{\sqrt{1 + (\omega_c RC)^2}} &= \frac{1}{\sqrt{2}} \\ \Rightarrow \sqrt{1 + (\omega_c RC)^2} &= \sqrt{2} \\ \Rightarrow 1 + (\omega_c RC)^2 &= 2 \\ \Rightarrow (\omega_c RC)^2 &= 1 \\ \Rightarrow \omega_c &= \frac{1}{RC} \end{aligned}$$


We can therefore say that the resistance for the desired cutoff frequency is $R = 1/\omega_c C$, and since $\omega_c = 2\pi \cdot f_c$, it is equivalent to saying

$$\begin{aligned} R &= \frac{1}{2\pi \cdot f_c \cdot C} \\ &= \frac{1}{2\pi \cdot 200[Hz] \cdot 22[nF]} \\ &= \frac{10^7}{\tau \cdot [Hz] \cdot 44[F]} \\ &\approx 36.2k\Omega \end{aligned}$$

□


“ For the value you have found for R , and a capacitor value of $C = 22\text{nF}$, use Matlab and plot the ratio of the amplitude of the input signal to the amplitude of the output signal ($|H(j\omega)|$), for frequencies in the range 0-20kHz. ”

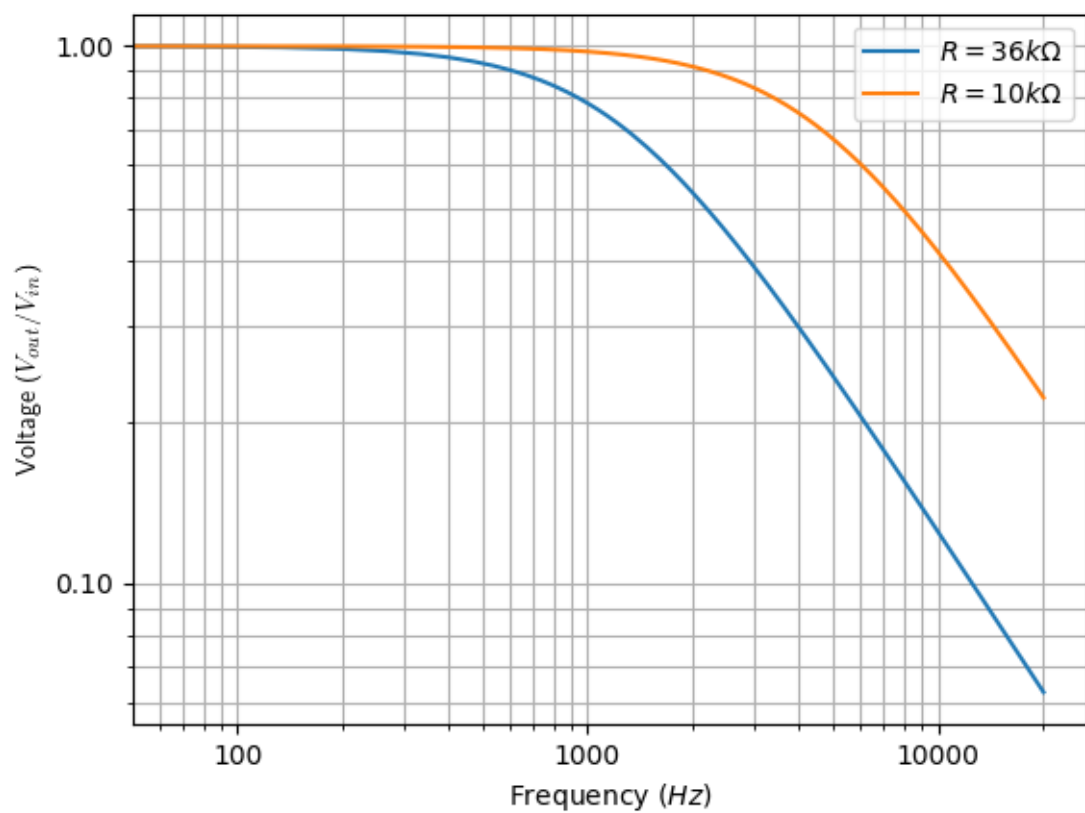“ Do the same for $R = 10\text{k}\Omega$ and combine the two curves together in a single plot. ”



□

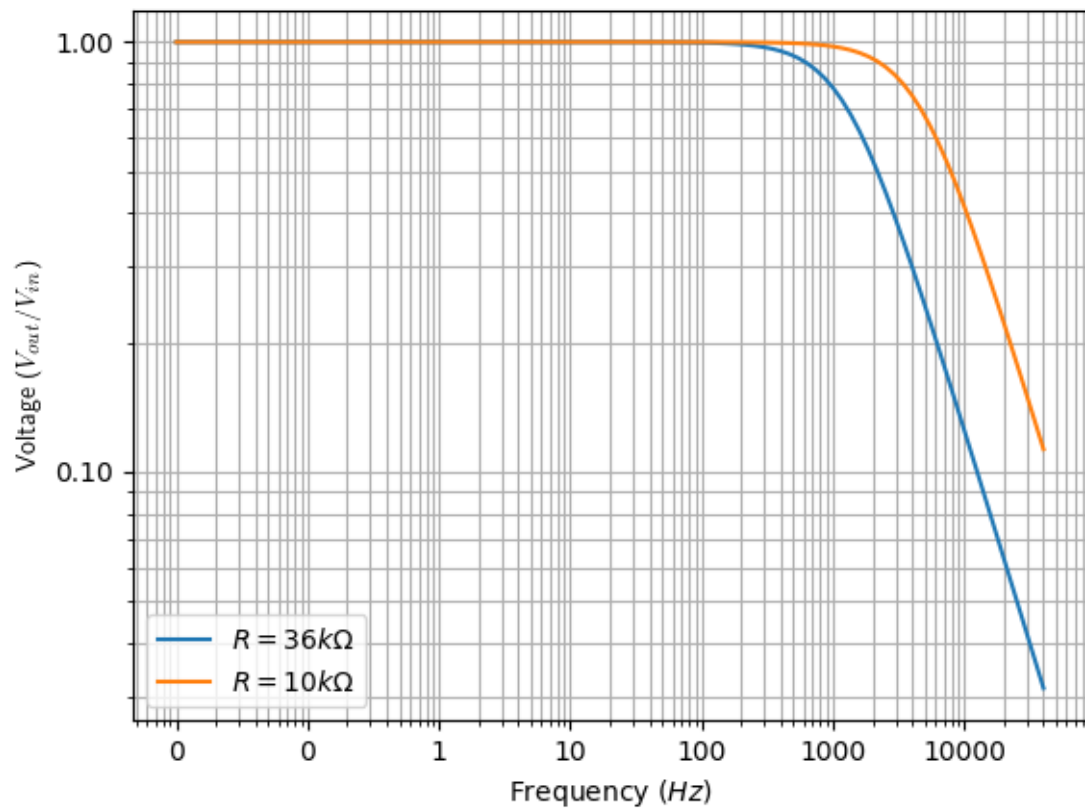“
Make an new plot of the curves found in question 4/5 using logarithmic axes by replacing "plot()" with "loglog()" in Matlab. Follow with the command "ylim([0.01 2])" and "grid on", to get a better view
”



□

Submitted by Rolf Vidar Hoksas on March 6, 2020.